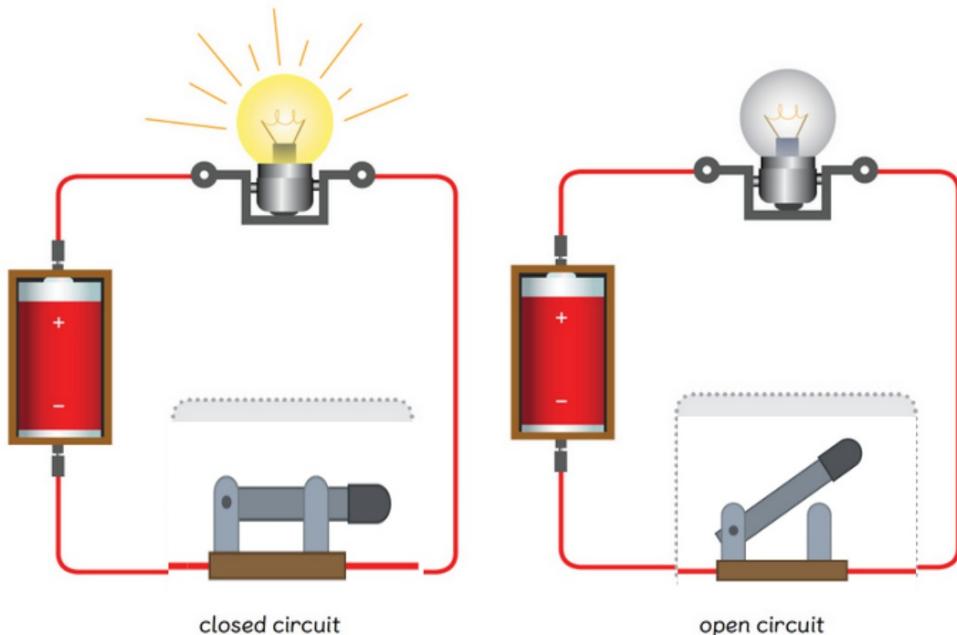





Use the stickers at the back of the book to complete the circuits.

Student's Book p.125



Check Your Learning

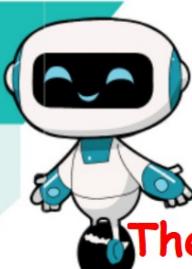What happens to the lamp if there is a break in the electrical circuit?



The lamp will not light up.