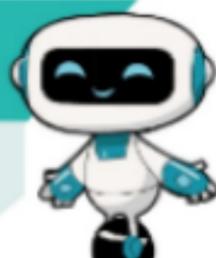


Check Your Learning

What are some ways to change the brightness of a lamp in a circuit?



1. changing the number of cells
2. changing the number of light bulbs
3. changing the length of the wires